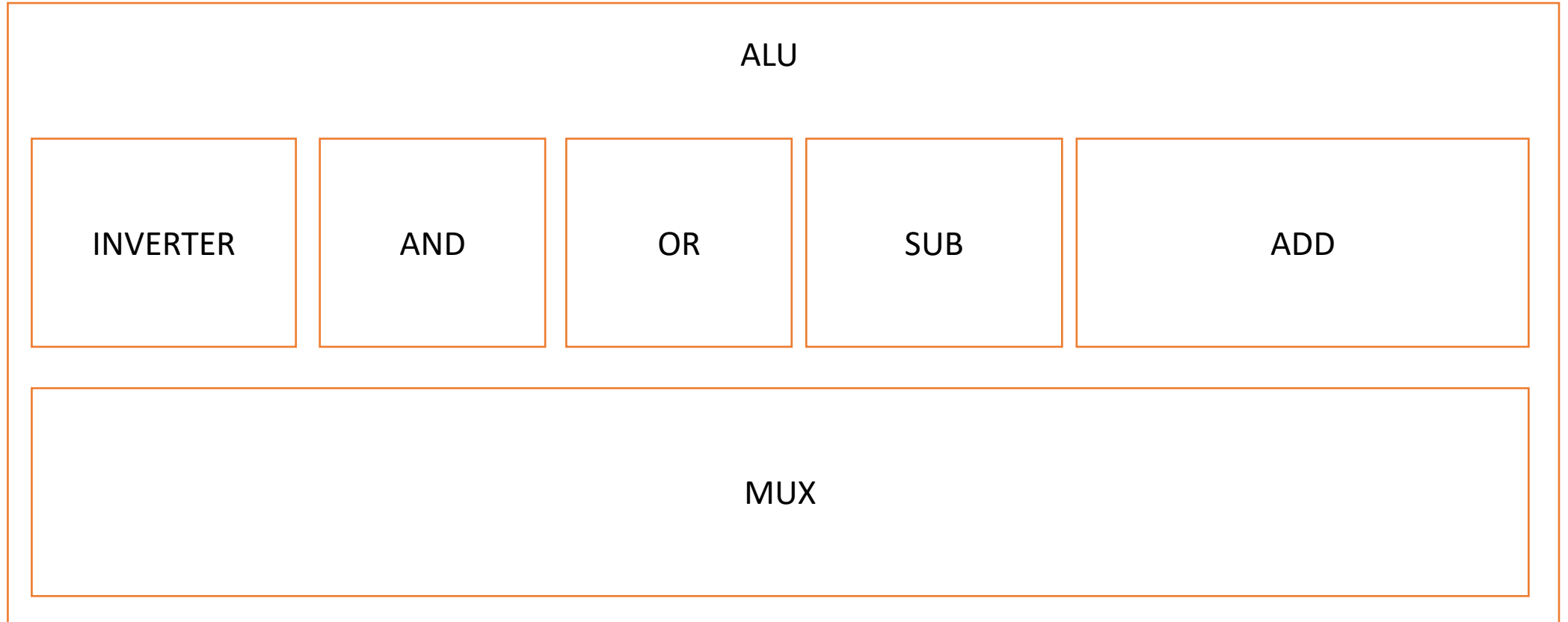





8-Bit ALU

Physical layout and pre-layout simulation



ALU - architectural top view




ALU - physical top view

   


INVERTER 8-bit

 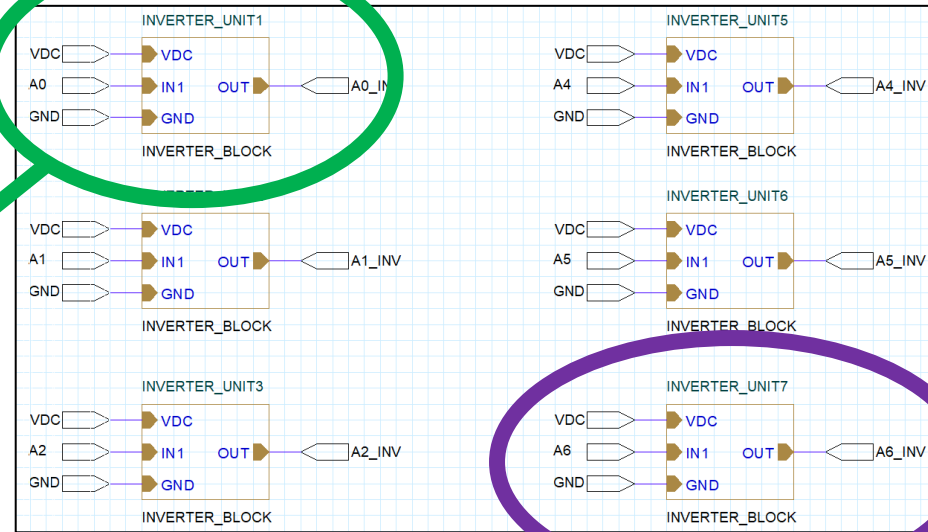




AND 8-bit

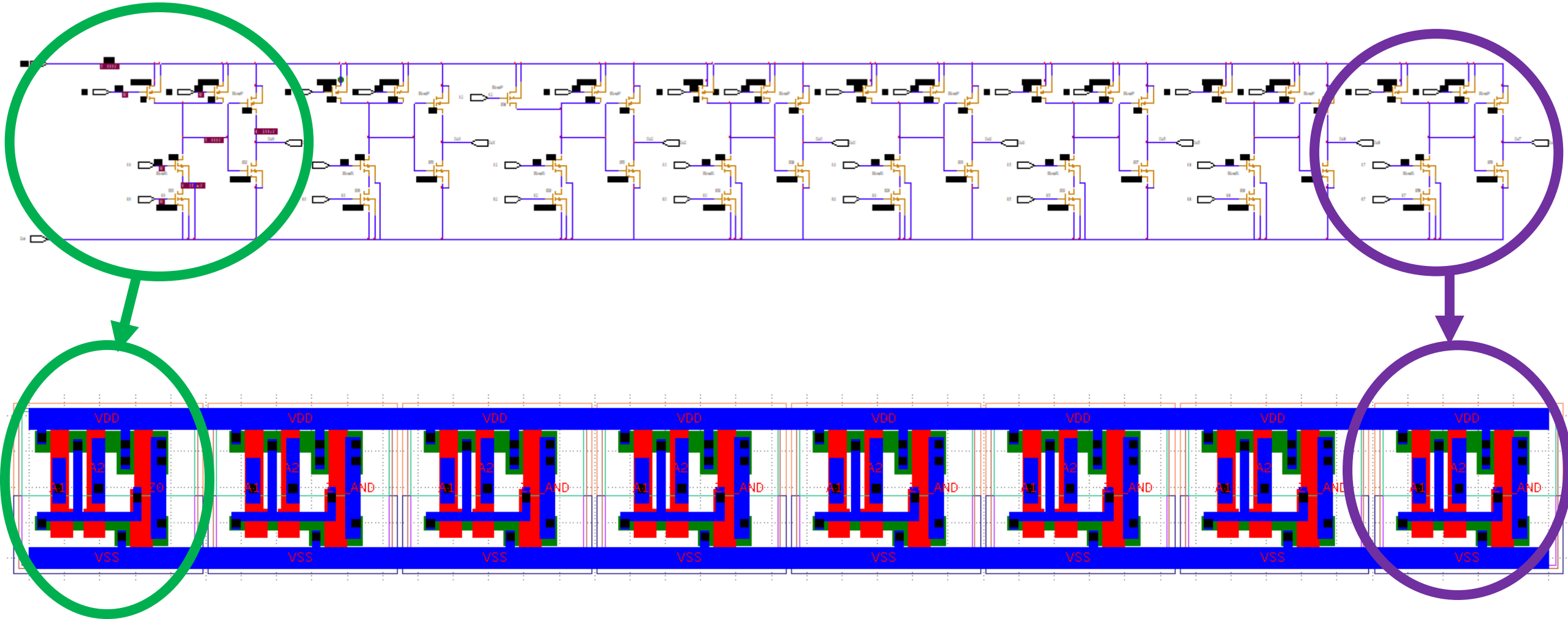


OR 8-bit

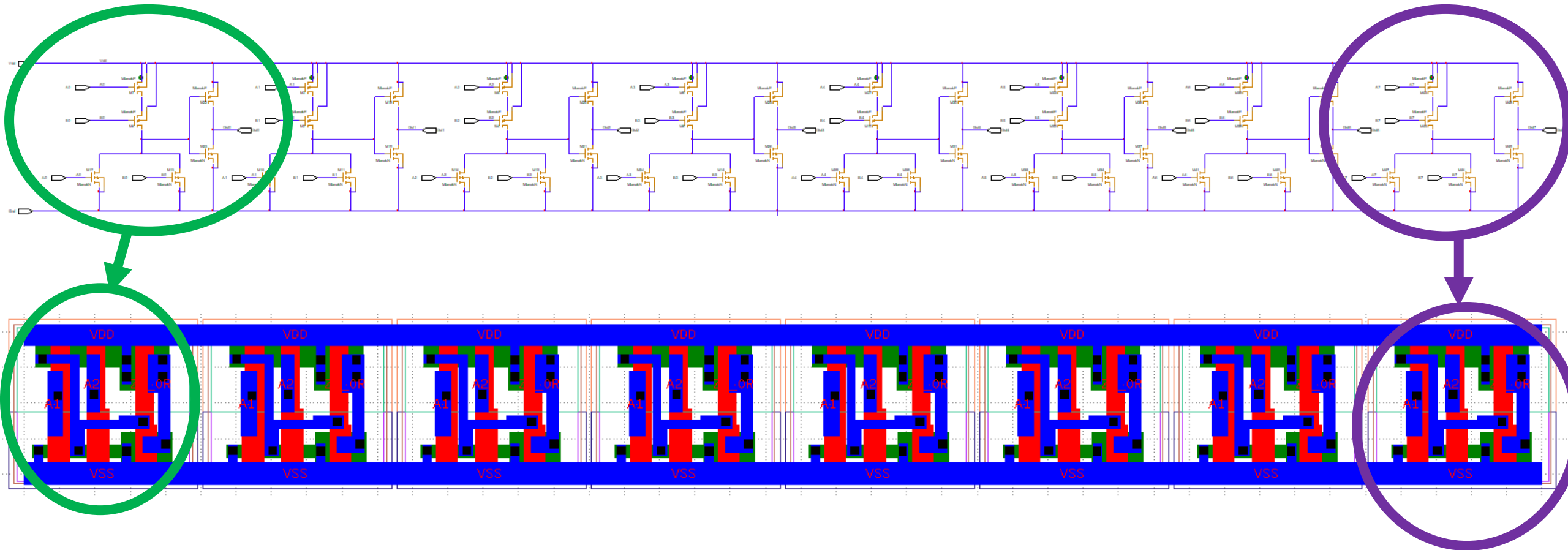


SUBTRACTOR 8-bit (Pseudo subtractor?)

 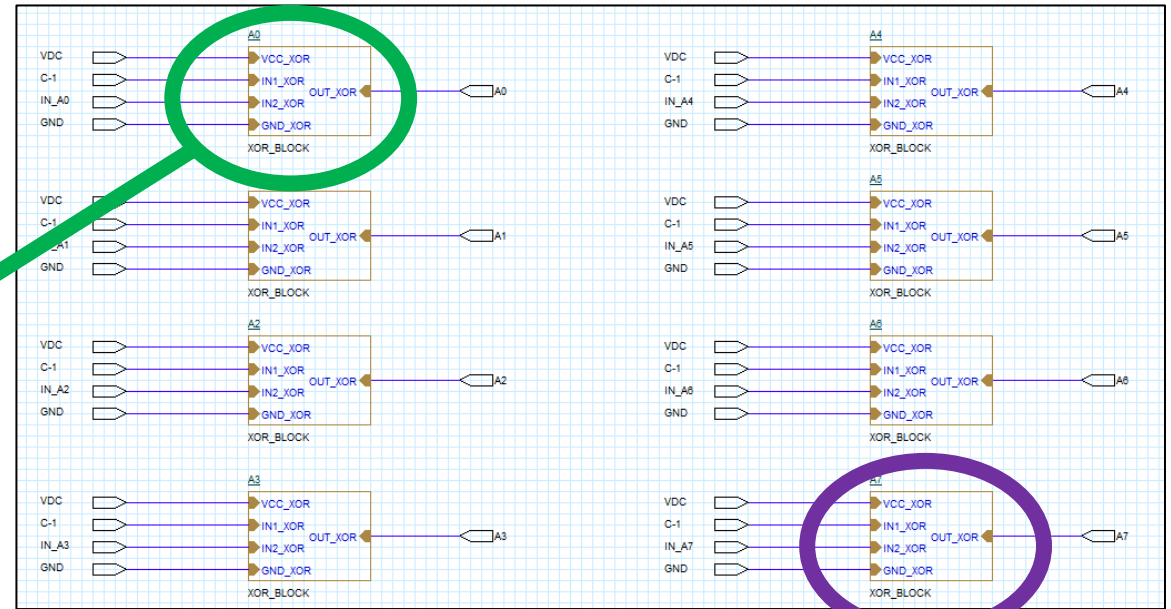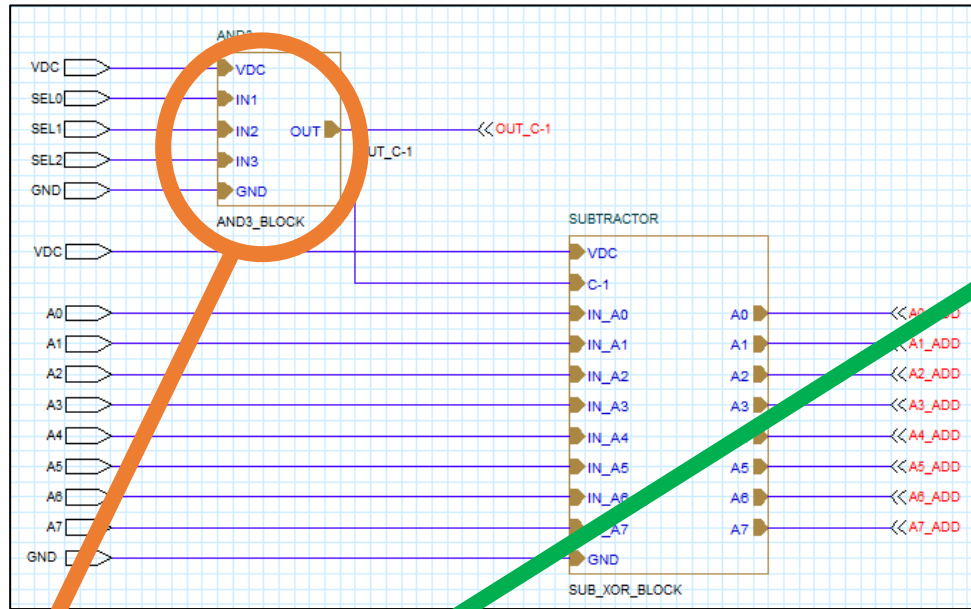


ADDER 8-bit

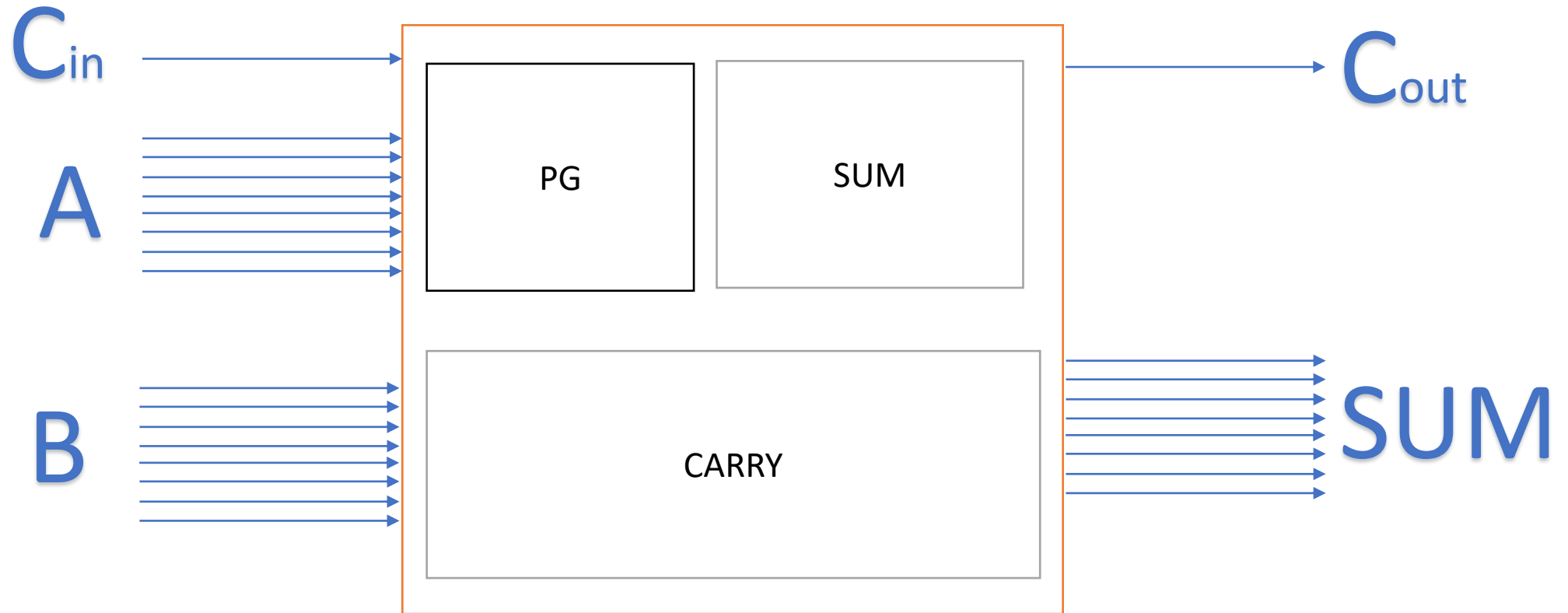


Propagate and Generate 1-bit

 


Propagate-Generate 4-bit

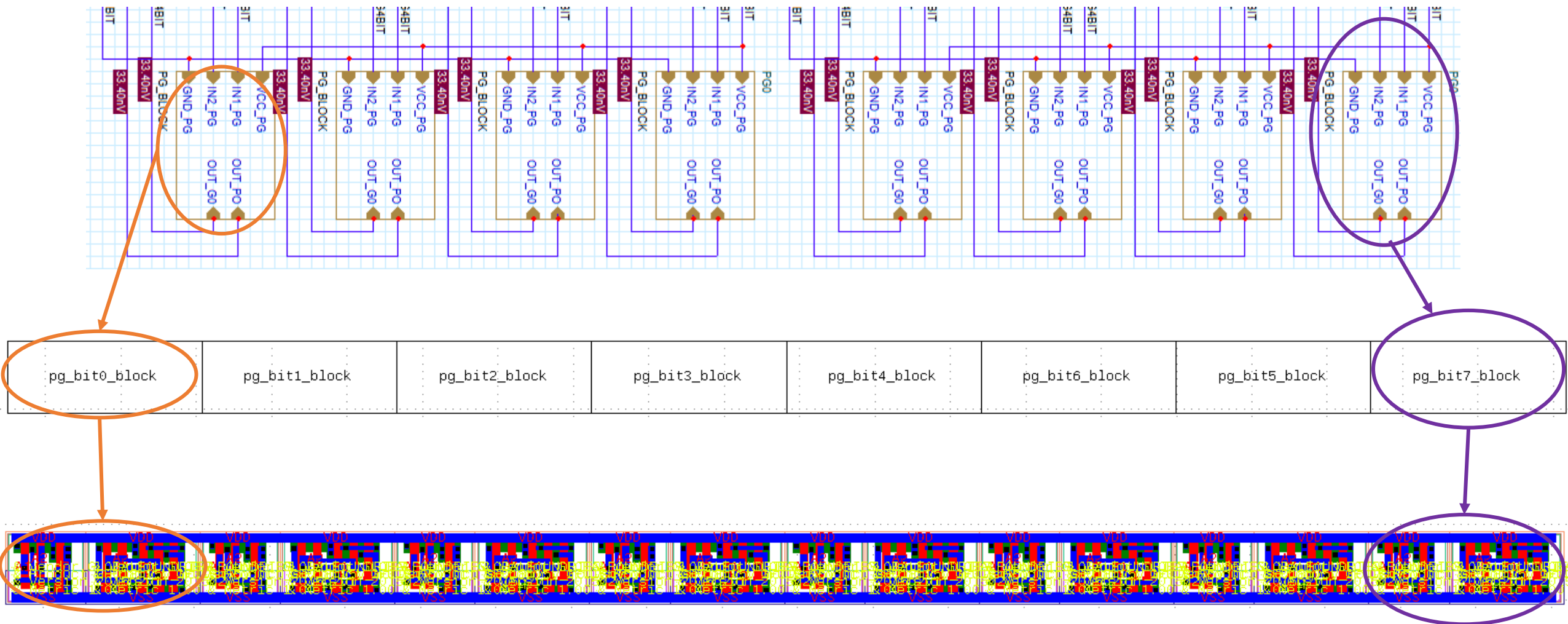


Carry Generator 4-bit

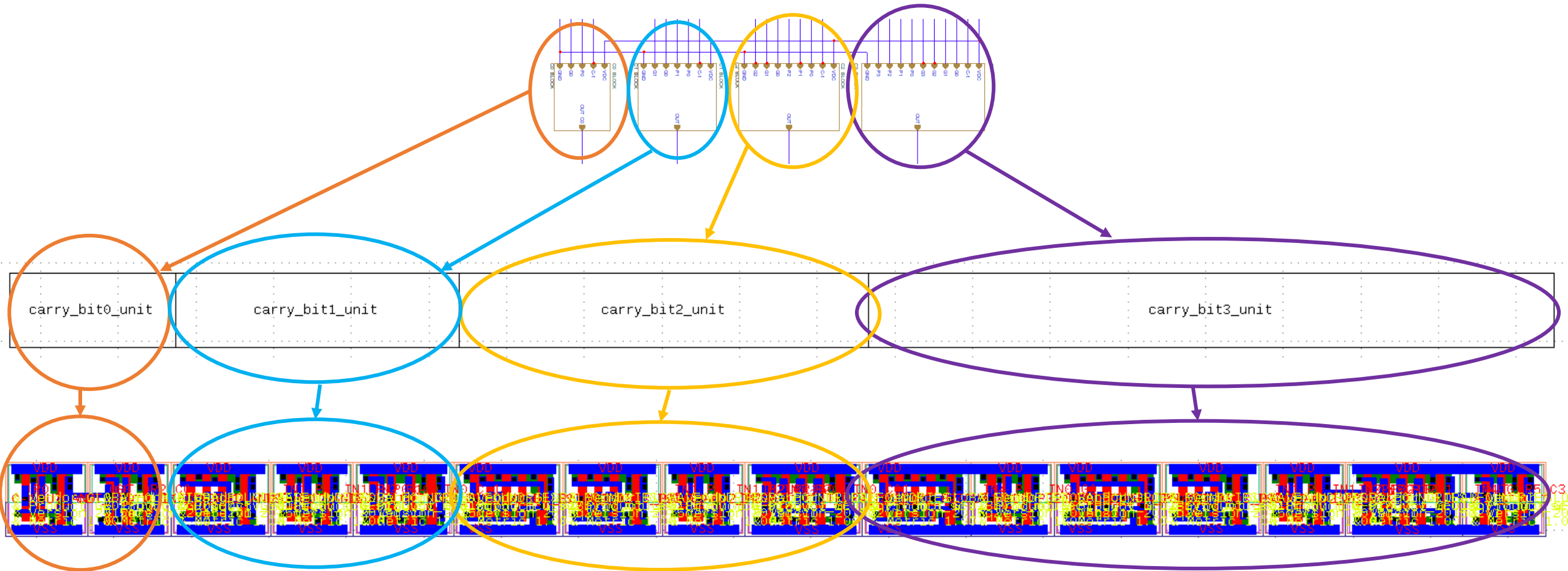


Carry Generator 8-bit

 

Sum 8-bit

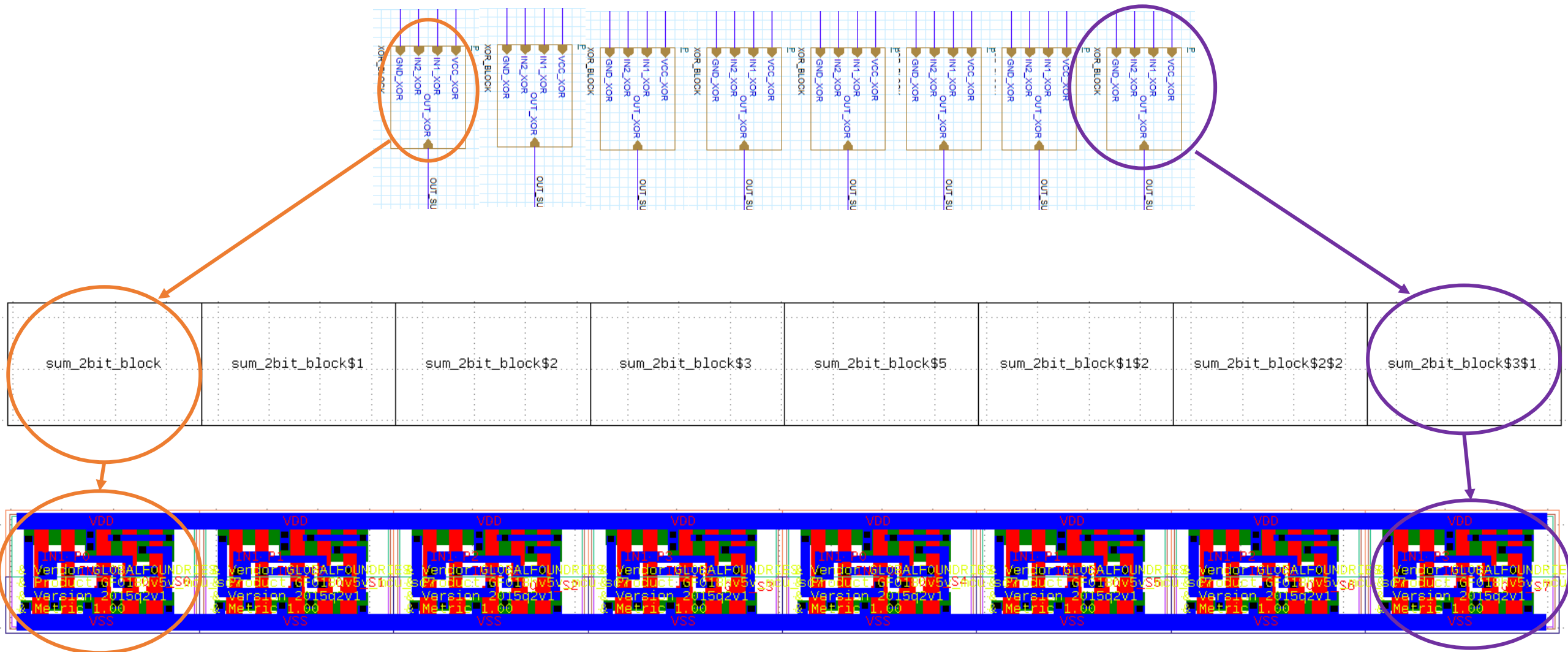

Adder 8-bit

 

MUX

000->INVERT

100 -> NOP

010 -> OR



110 -> NOP

001 -> AND



101 -> NOP

011 -> ADD


111 -> SUB

  


MUX 2x1

  

MUX 8x1

 


mux_2bit_block	mux_2bit_block\$1	mux_2bit_block\$2	mux_2bit_block\$3	mux_2bit_block\$4	mux_2bit_block\$5	mux_2bit_block\$6	mux_2bit_block\$14


 





Area

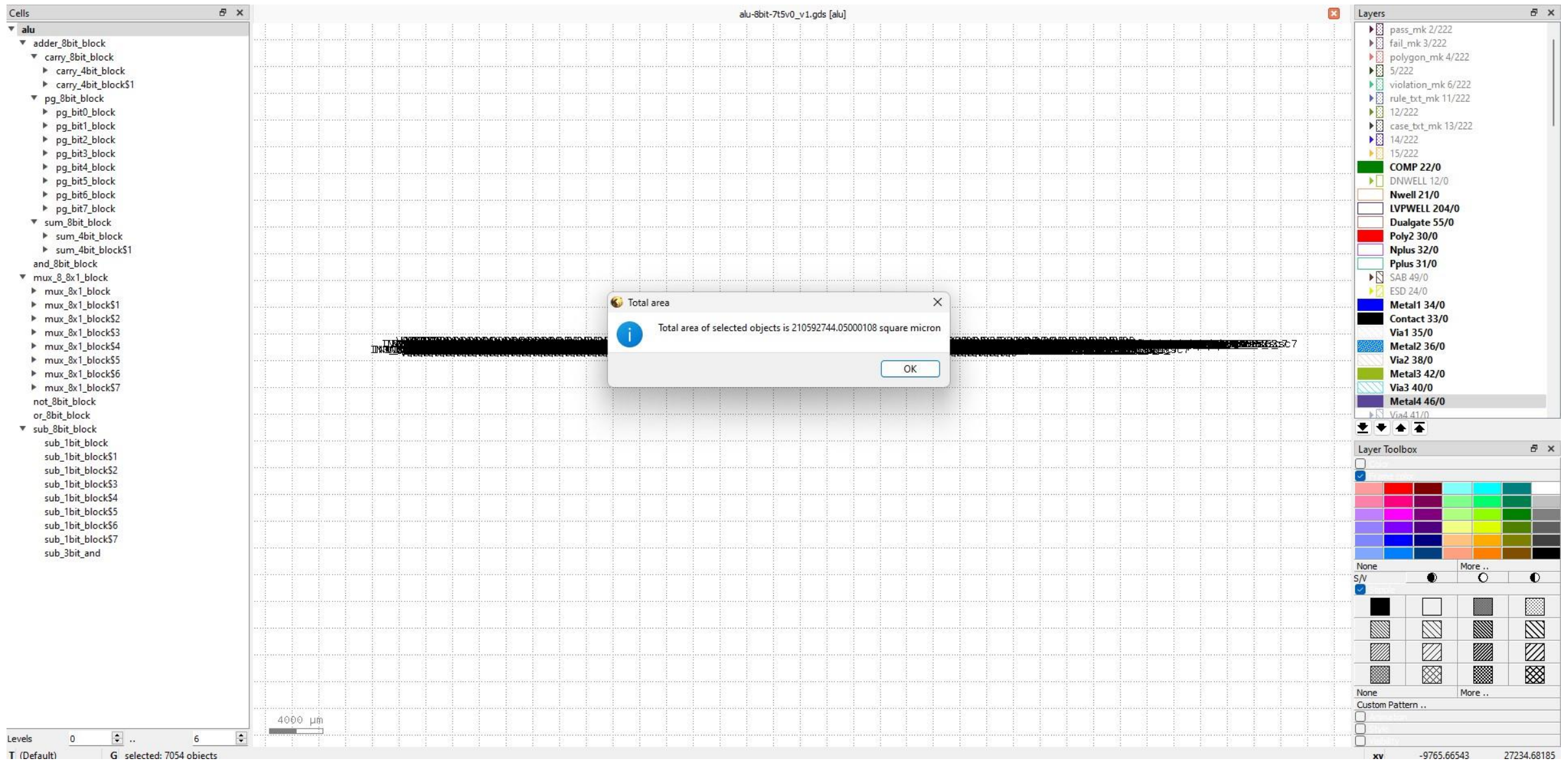

Complete ALU

 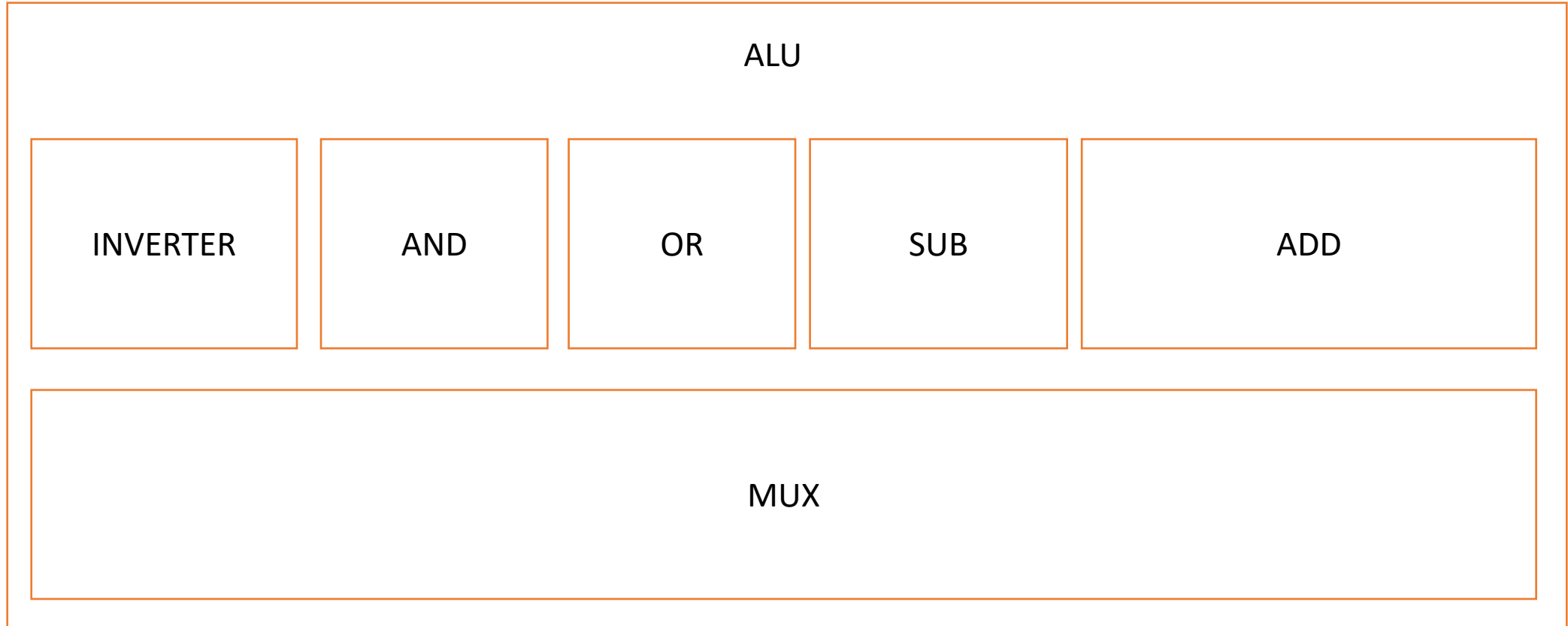


Test setup

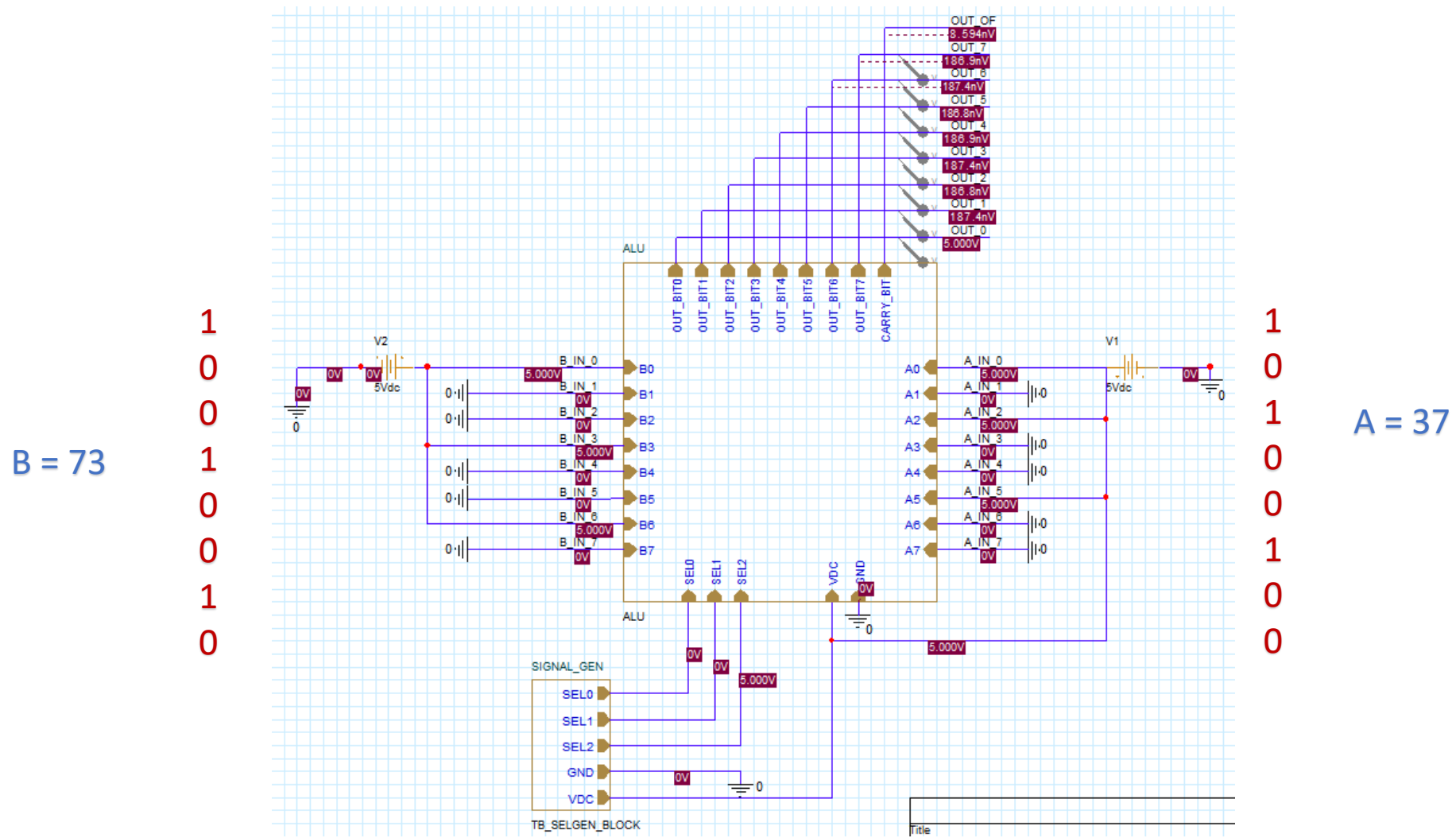


Input data configuration and output

BIT	7	6	5	4	3	2	1	0
B=37	0	0	1	0	0	1	0	1
A=73	0	1	0	0	1	0	0	1
G	0	0	0	0	0	0	0	1
P	0	1	1	0	1	1	0	0
C0								1
C1							0	
C2						0		
C3					0			
C4				0				
C5			0					
C6		0						
C7	0							
INVERT(EXP)	1	0	1	1	0	1	1	0
INVERT(OBSERVED)	1	0	1	1	0	1	1	0
ADD (EXP)	0	1	1	0	1	1	1	0
ADD (OBSERVED)	0	1	1	0	1	1	1	0
SUB (EXP)	0	0	1	0	0	1	0	0
SUB (OBSERVED)	0	0	1	0	0	1	0	0
OR (EXP)	0	1	1	0	1	1	0	1
OR (OBSERVED)	0	1	1	0	1	1	0	1
AND(EXP)	0	0	0	0	0	0	0	1
AND (OBSERVED)	0	0	0	0	0	0	0	1


SELECT Signals

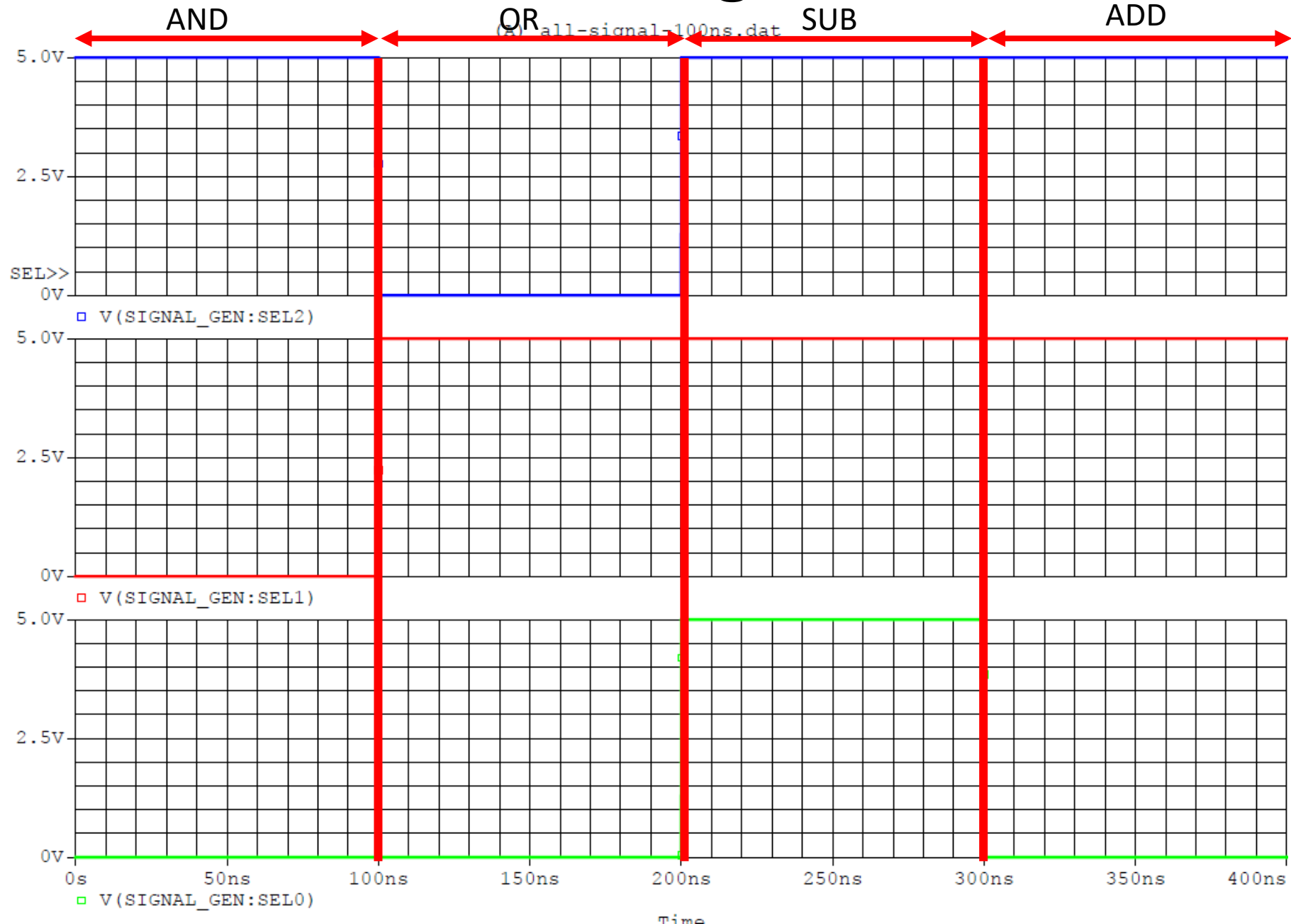




 

Critical path

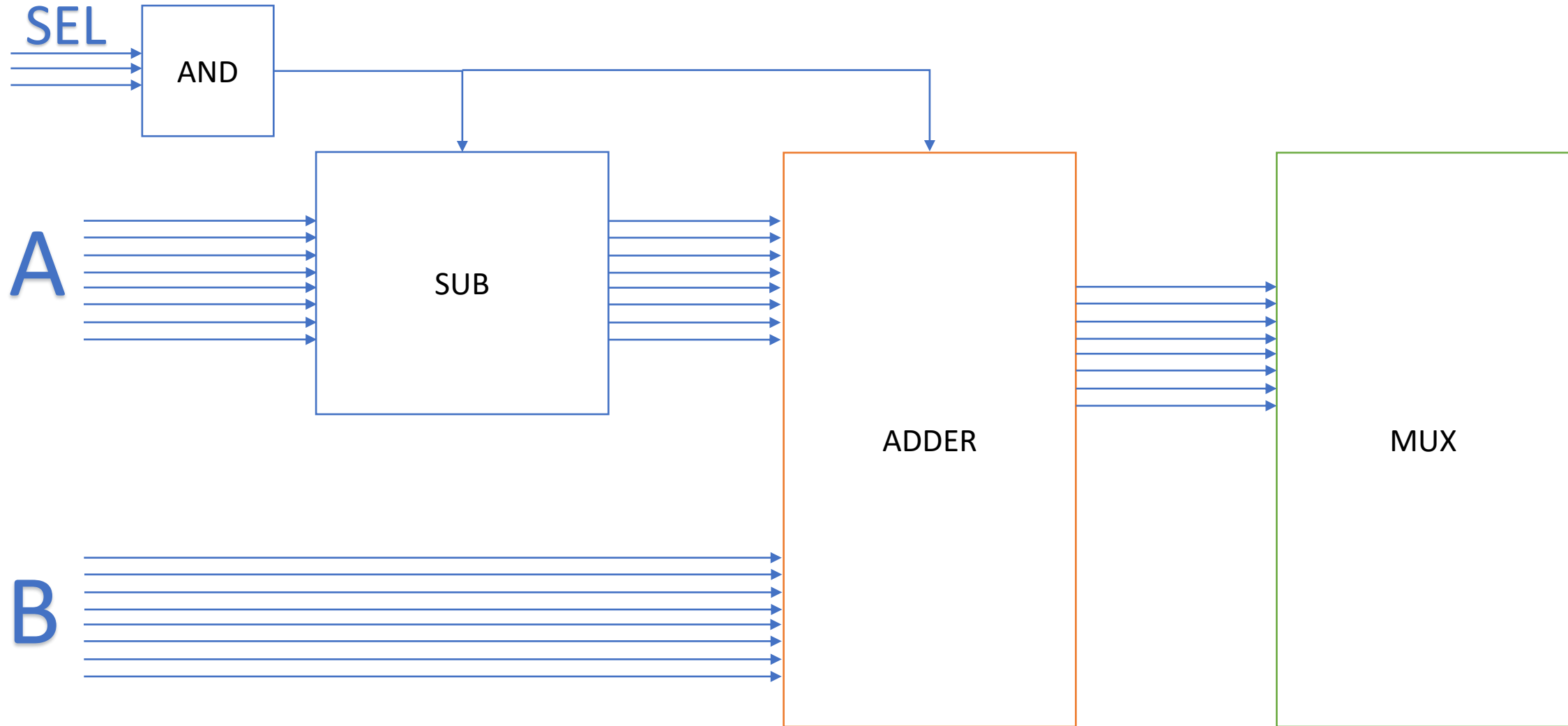

Ripple carry vs Carry Lookahead

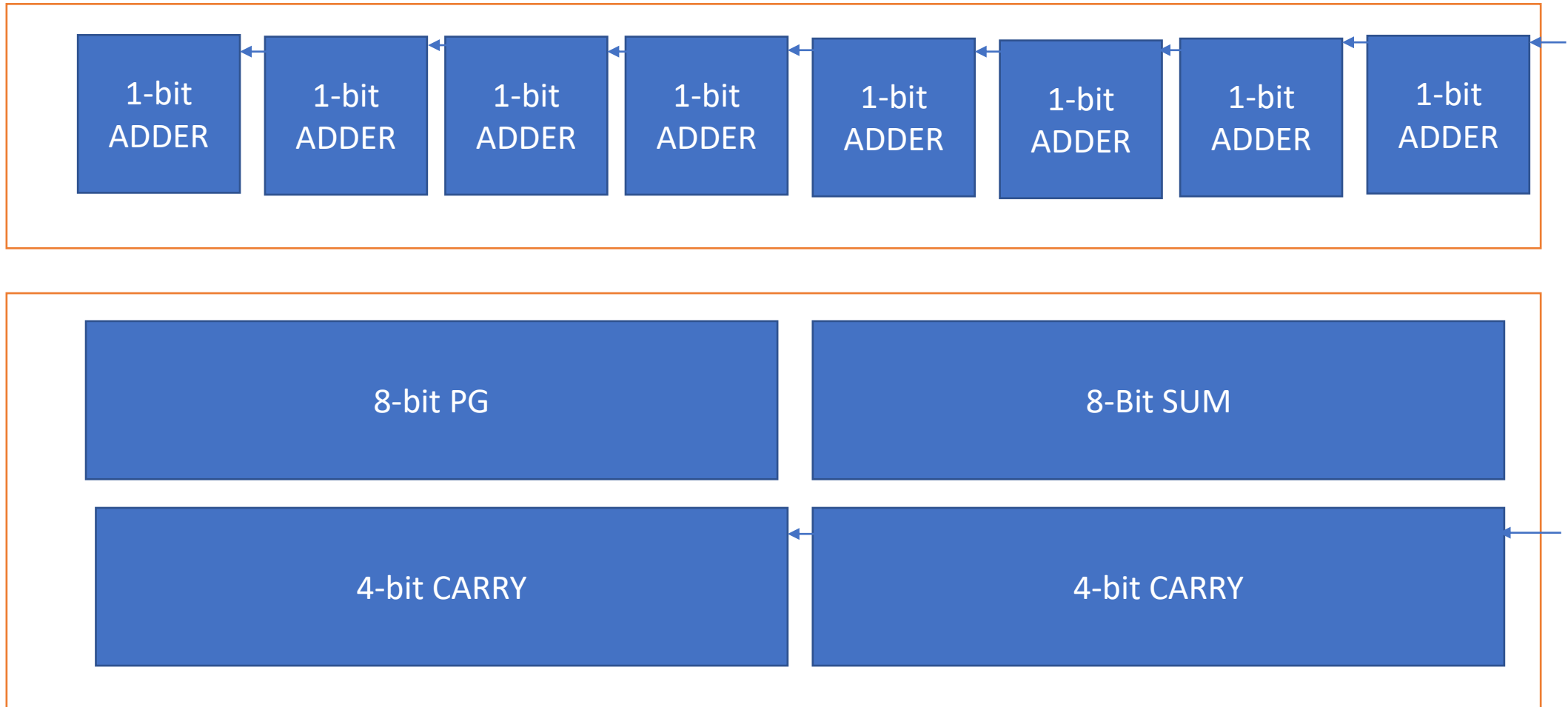

Thank you

ELEG/CPEG 448